

# A Broadband Zero-IF Down-Conversion Mixer in 130 nm SiGe BiCMOS for Beyond 5G Communication Systems in D-Band

Andreas Tsouchlos | 10.09.2024




# Overview

- Proposed Ideas
- Own Simulations
- Discussion & Conclusion

- Proposed Ideas
- Own Simulations
- Discussion & Conclusion

## Proposed Design: Overview

- Paper by Maiwald, *et al.* [Mai+21]

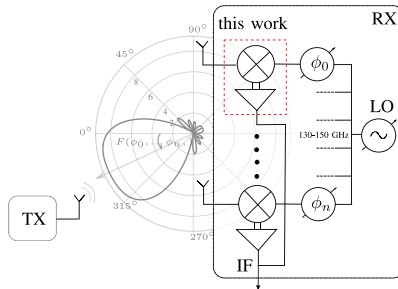


- High bandwidth, low power consumption, small size
- Applicable to electronic beam steering for mm-Wave
- SiGe BiCMOS technology (B11HFC) from Infineon Technologies AG with  $f_t/f_{max}$  of 250/370 GHz

[Mai+21] T. Maiwald et al., "A Broadband Zero-IF Down-Conversion Mixer in 130 nm SiGe BiCMOS for Beyond 5G Communication Systems in D-Band", in *IEEE Transactions on Circuits and Systems II: Express Briefs*, vol. 68, no. 7, pp. 2277-2281, July 2021

# Proposed Design: Mixer Core Cell


- Usage of switching quad (SQuad) instead of conventional Gilbert cell for more voltage headroom
- Mixer loaded by modified Cherry-Hooper [CH63] transimpedance amplifier (TIA)
- Transmission line based differential L-type matching networks for high bandwidth
- Signal fed using marchand baluns for high bandwidth

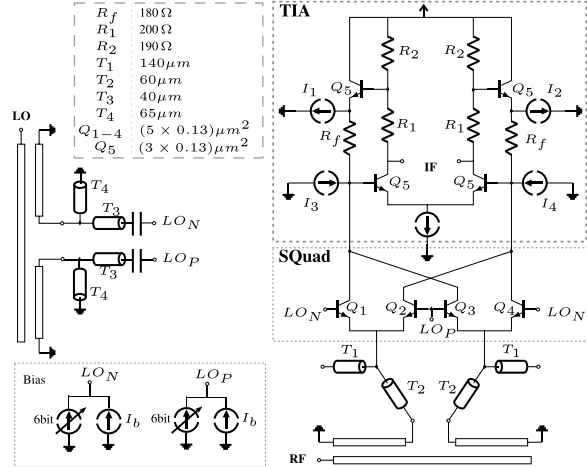





[CH63] E.M. Cherry and D.E. Hooper, "The design of wide-band transistor feedback amplifiers", *Proceedings of the Institution of Electrical Engineers*, vol. 110, pp. 375-389, February 1963
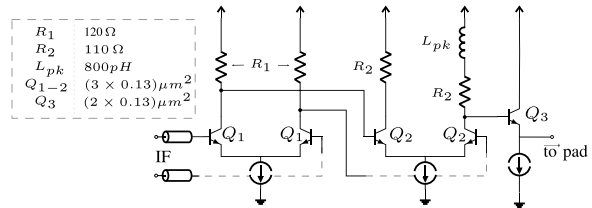
# Proposed Design: IF Buffer

- Three-stages: two differential amplifier stages and an emitter follower
- Includes differential to single-ended conversion enabling dense chip-to-package transition
- Inductive peaking for bandwidth enhancement


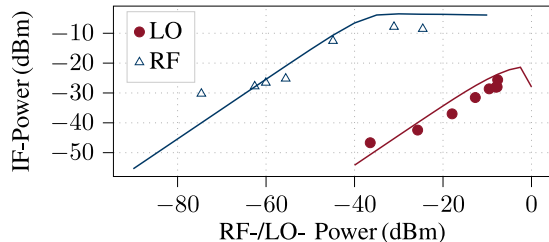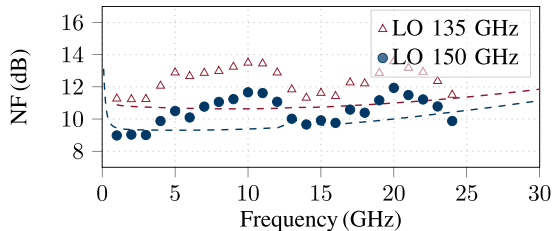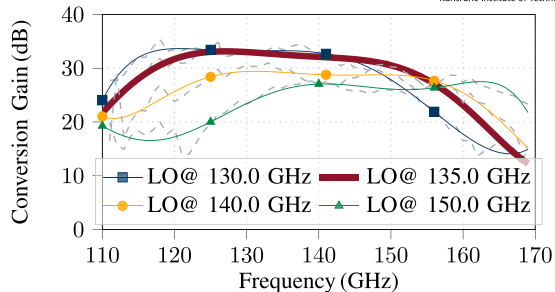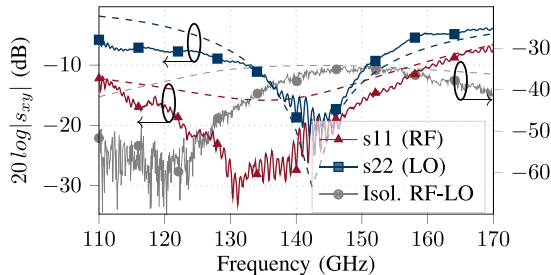
# Proposed Design: Simulation/Measurement Results



■ Proposed Ideas

■ Own Simulations

■ Discussion & Conclusion



- 1 Determination of operating point of individual stages
  - SQuad
  - TIA
  - Buffer
- 2 Integration
  - SQuad & TIA
  - SQuad, TIA & Buffer
- 3 Further iterative optimization of parameters (e.g., determine LO power, increase buffer current for linearity, ...)
- 4 Matching of input and output


# Operating Point: Switching Quad

## ■ Operation

- Responsible for actual mixing
- Multiplication of RF-signal with square wave  
→ generation of mixing products at IF-frequency and harmonics


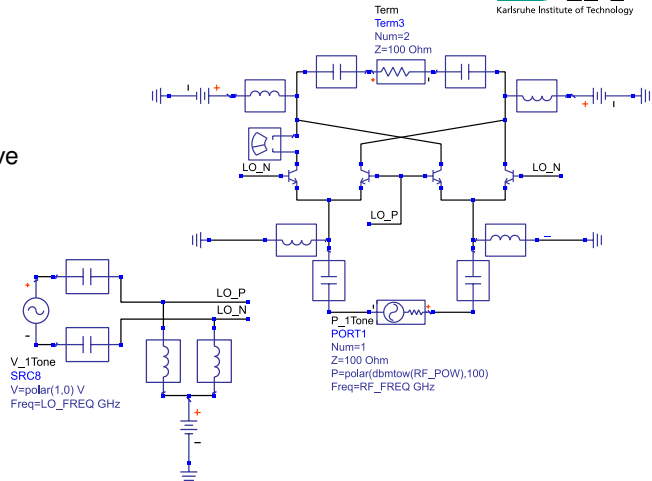
## ■ Determination of operating point

- Exact value of  $V_{CE}$  not crucial
- $V_{BE}$ : Examination of  $s_{21}$  of Large-signal s-parameter simulation and noise figure (analogous to [Mai+21])



[Mai+21] T. Maiwald et al., "A Broadband Zero-IF Down-Conversion Mixer in 130 nm SiGe BiCMOS for Beyond 5G Communication Systems in D-Band", in *IEEE Transactions on Circuits and Systems II: Express Briefs*, vol. 68, no. 7, pp. 2277-2281, July 2021

# Operating Point: Switching Quad

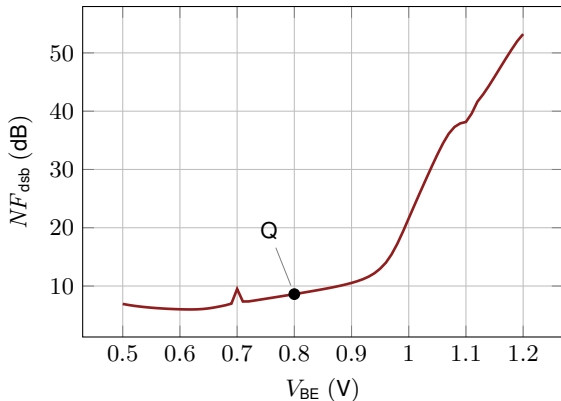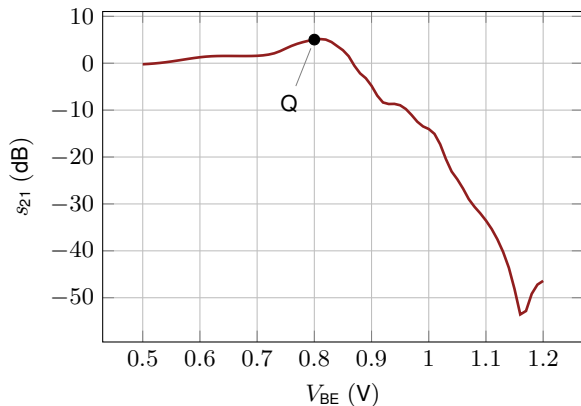

- Plotted for  $f_{LO} = 135$  GHz,  $f_{RF} = 140$  GHz
- Double-sideband noise figure  $NF_{dsb}$  (direct conversion mixer)
- Chosen operating point:  $V_{BE} = 0,8$  V


# Operating Point: Transimpedance Amplifier

## ■ Operation



- Conversion of switched current to voltage, amplification
- Modified Cherry-Hooper topology: decoupling of bandwidth and gain, modification for greater dynamic range
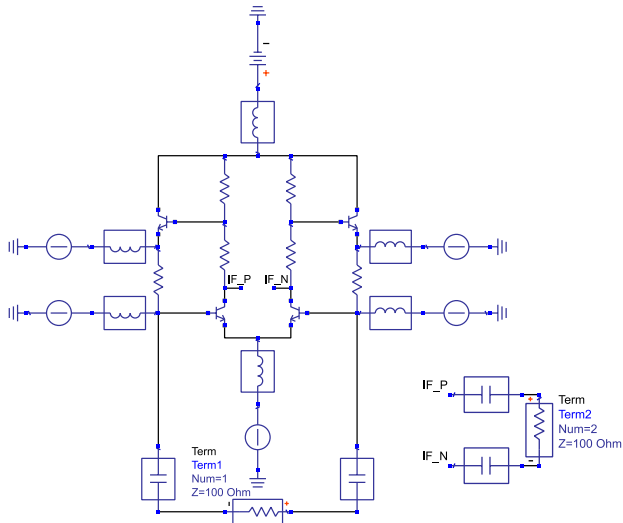
## ■ Determination of operating point

- Exact value of supply voltage not crucial
- S-parameter simulation: Examination of maximum available gain ( $MAG$ ) and minimum noise figure ( $NF_{min}$ )
- At this stage: only determination of operating point of bottom transistors


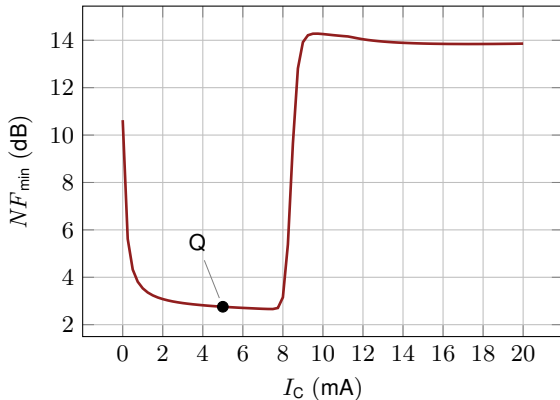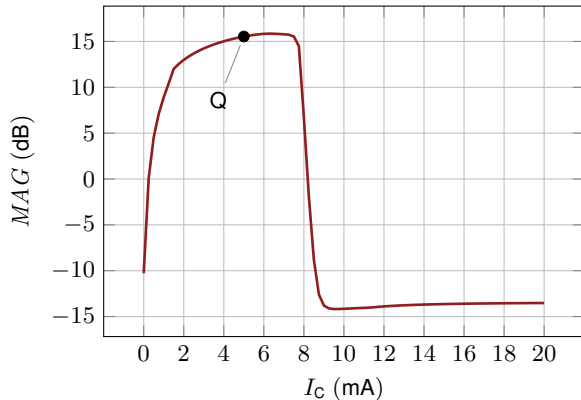
# Operating Point: Transimpedance Amplifier



- Plotted for  $f_{IF} = 20$  GHz
- Chosen operating point:  $I_C = 5$  mA (with multiplier of 10)


# Operating Point: Buffer

## ■ Operation



- Amplification of signal
- Comprises three stages: two differential amplifiers and an emitter follower
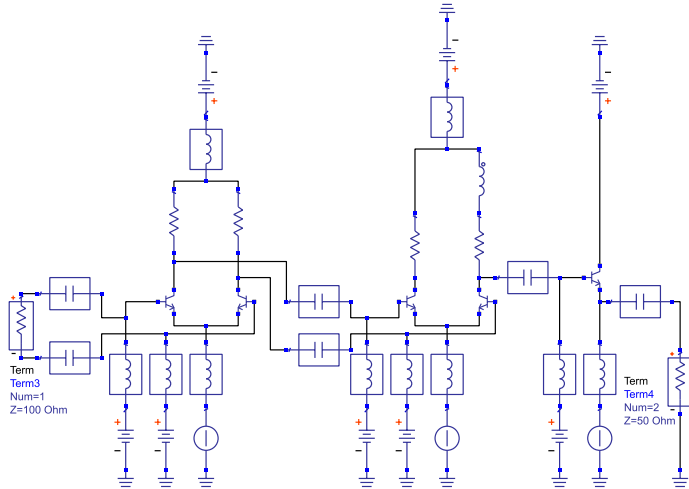
## ■ Determination of operating point

- Exact value of supply voltage not crucial at this point
- S-parameter simulation: Examination of  $MAG$  and  $NF_{min}$
- **Note:** Adjustment with respect to linearity at the very end




# Operating Point: Buffer

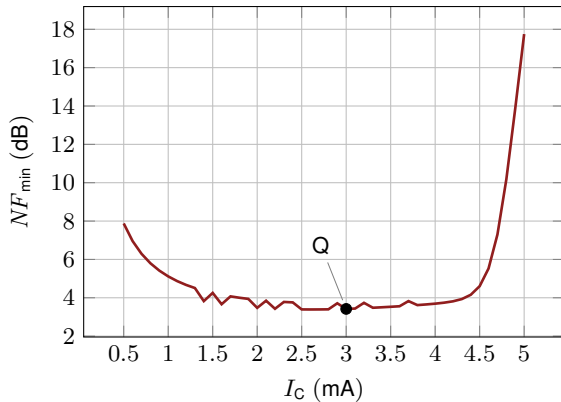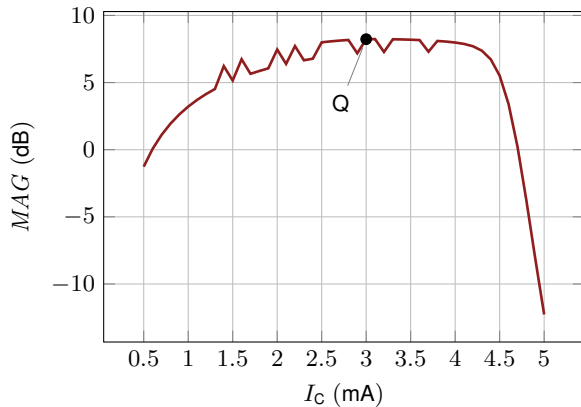

- Plotted for  $f_{IF} = 20$  GHz
- Chosen operating point:  $I_C = 3$  mA




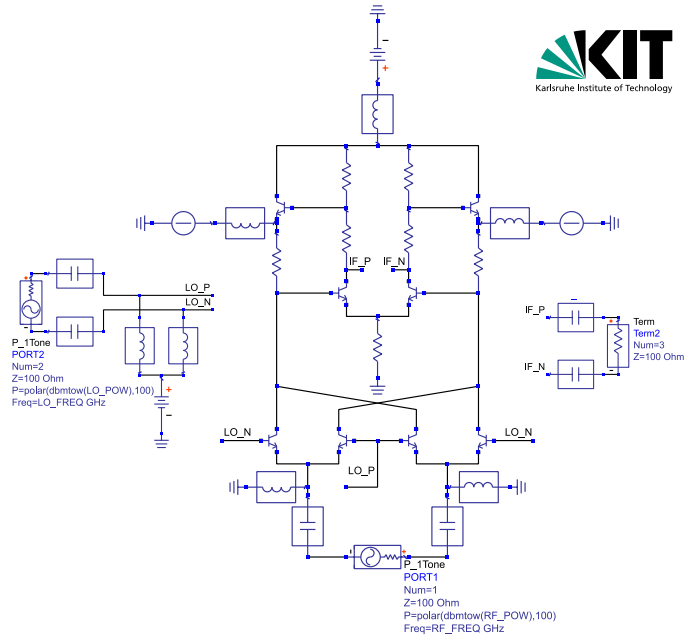
# Integration: SQuad & TIA

- DC coupling → Redesign of bias circuitry
- Supply voltage fixed to 2,5 V to not exceed breakdown voltage of transistors
- Examination using Harmonic-Balance simulation:
  - Conversion gain
  - 1 dB compression point ( $P_{1\text{ dB}}$ )






# Integration: SQuad & TIA

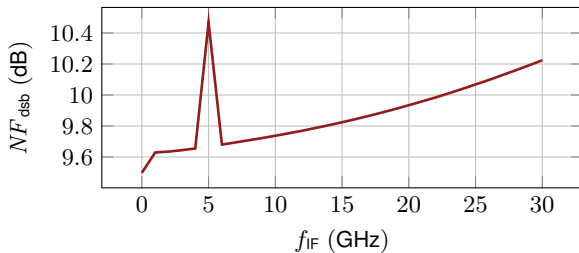
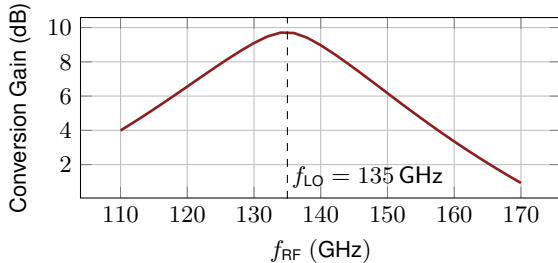
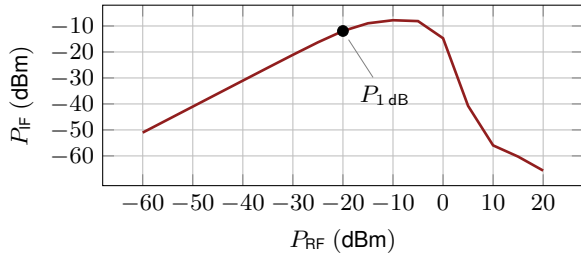
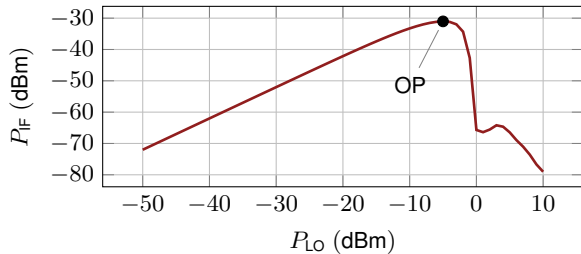

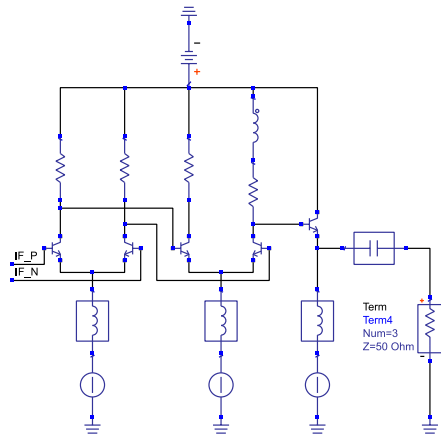
# Integration: SQuad, TIA & Buffer



- DC coupling → Redesign of bias circuitry
- Supply voltage fixed to 2,5 V
- Examination using Harmonic-Balance simulation:
  - Conversion gain
  - 1 dB compression point ( $P_{1\text{ dB}}$ )







# Integration: SQuad, TIA & Buffer

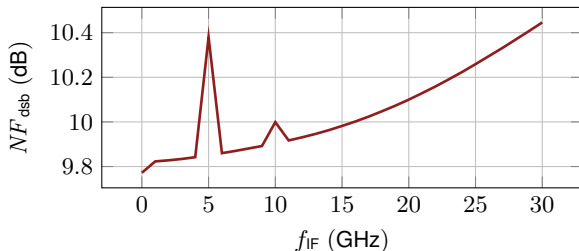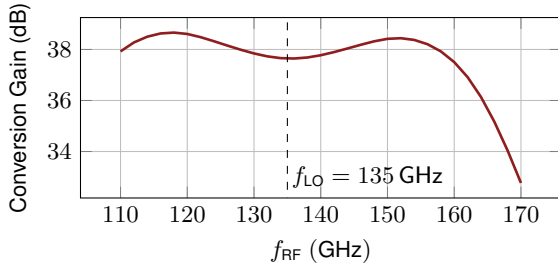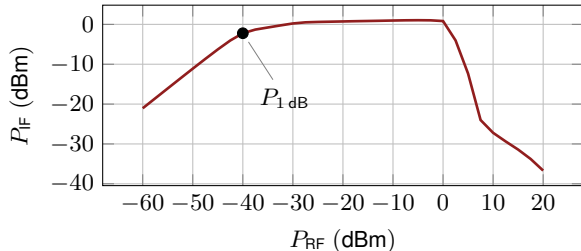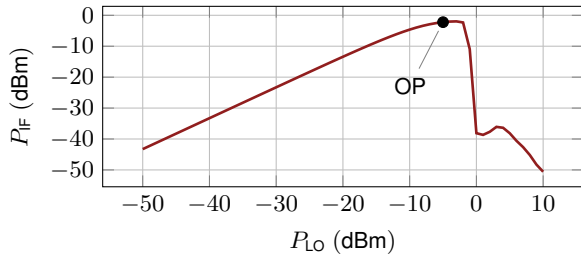

# Final Circuit

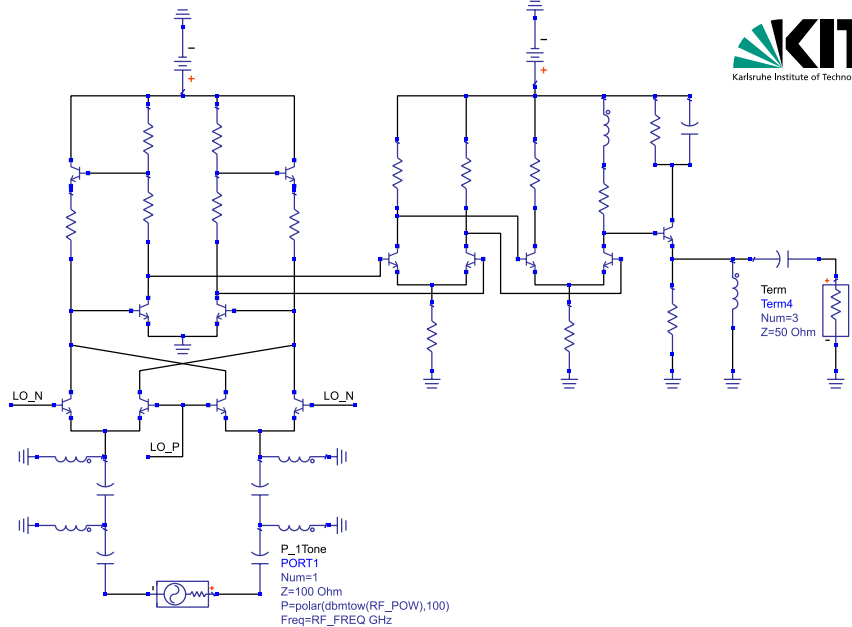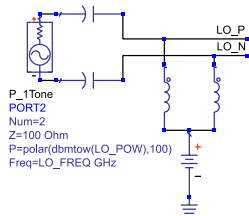

# Final Circuit

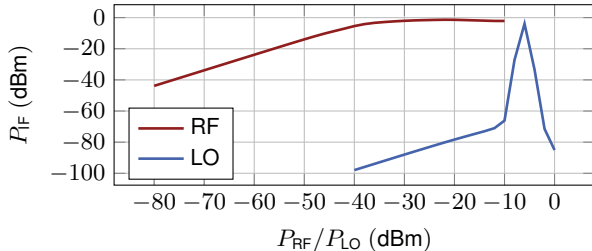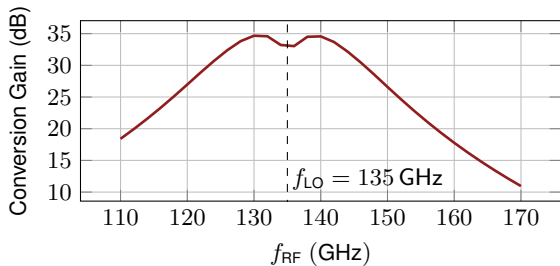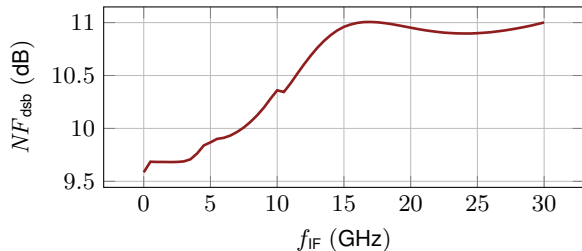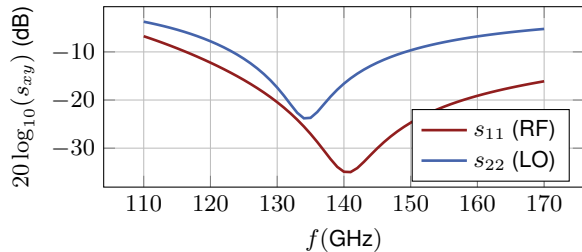

- Proposed Ideas
- Own Simulations
- Discussion & Conclusion

## ■ General structure

- Removal of  $g_m$  stage of Gilbert cell → more voltage headroom
- High bandwidth TIA and inductive peaking → high bandwidth
- Differential to single-ended conversion → dense chip-to-package transition

## ■ Own simulations

- Better results to be expected (technology with higher  $f_t$ ,  $f_{max}$ , stability not considered)
- Further investigation needed to determine whether unusual LO power behavior is problematic
- Maybe better results by using current mirrors to set operating points of buffer instead of resistors
- Maybe better results by replacement of discrete component matching networks by transmission line based ones

## ■ Applications of this design

- SiGe HBT technology integrable with CMOS → scalable, suitable for mixed-signal ICs
- Ideal for electronic beam steering in mm-Wave applications (because of small size, moderate noise figure)

Thank you for your attention!  
Any questions?

