

A Broadband Zero-IF Down-Conversion Mixer in 130 nm SiGe BiCMOS for Beyond 5G Communication Systems in D-Band

Andreas Tsouchlos | 10.09.2024





Overview

- Proposed Ideas
- Own Simulations
- Discussion & Conclusion

- Proposed Ideas
- Own Simulations
- Discussion & Conclusion

Proposed Design: Overview

- Paper by Maiwald, *et al.* [Mai+21]

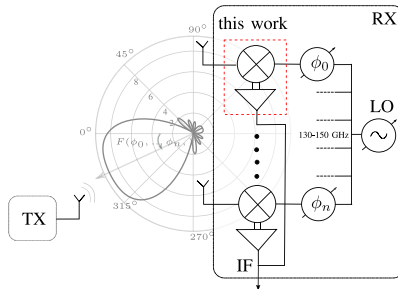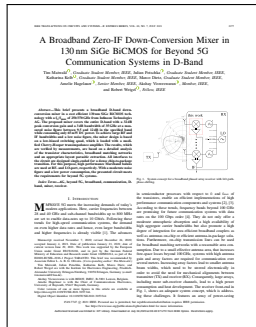


- High bandwidth, low noise figure, low power consumption, small size
- Applicable to electronic beam steering for mm-Wave
- 130nm SiGe BiCMOS technology from Infineon Technologies AG with f_t/f_{max} of 250/370 GHz

[Mai+21] T. Maiwald et al., "A Broadband Zero-IF Down-Conversion Mixer in 130 nm SiGe BiCMOS for Beyond 5G Communication Systems in D-Band", in *IEEE Transactions on Circuits and Systems II: Express Briefs*, vol. 68, no. 7, pp. 2277-2281, July 2021

Proposed Design: Mixer Core Cell


- Usage of switching quad (SQuad) instead of conventional Gilbert cell for more voltage headroom
- Mixer loaded by modified Cherry-Hooper [CH63] transimpedance amplifier (TIA)
- Transmission line based differential L-type matching networks for high bandwidth
- Signal fed using marchand baluns for high bandwidth

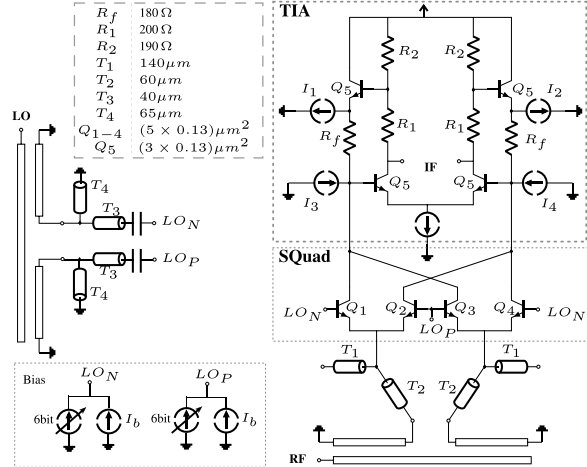





[CH63] E.M. Cherry and D.E. Hooper, "The design of wide-band transistor feedback amplifiers", *Proceedings of the Institution of Electrical Engineers*, vol. 110, pp. 375-389, February 1963

Proposed Design: IF Buffer

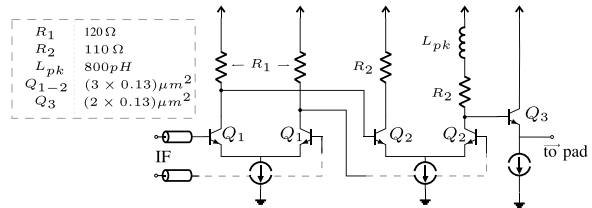- Three-stages: two differential amplifier stages and an emitter follower
- Includes differential to single-ended conversion enabling dense chip-to-package transition
- Inductive peaking for bandwidth enhancement



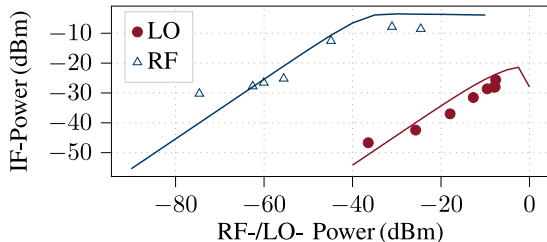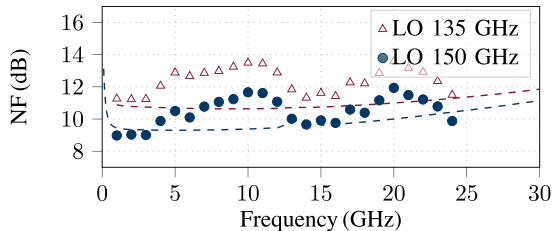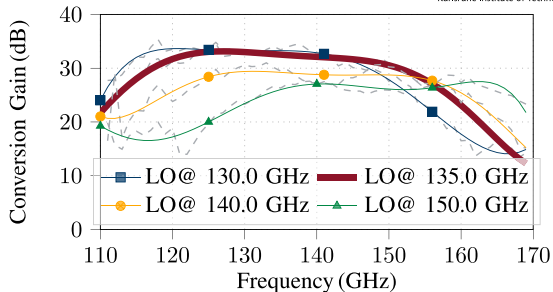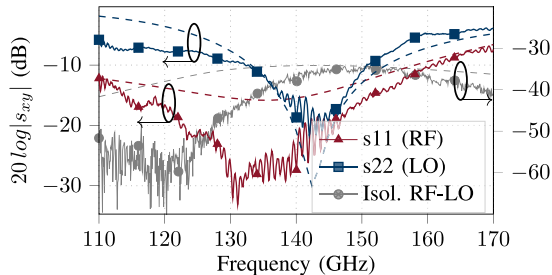Proposed Design: Simulation/Measurement Results



■ Proposed Ideas

■ Own Simulations

■ Discussion & Conclusion

- 1 Determination of operating point of individual stages
 - SQuad
 - TIA
 - Buffer
- 2 Integration
 - SQuad & TIA
 - SQuad, TIA & Buffer
- 3 Further iterative optimization of parameters (e.g., determine LO power, increase buffer current for linearity, ...)
- 4 Matching


Operating Point: Switching Quad

■ Operation

- Responsible for actual mixing
- Multiplication of RF-signal with square wave
→ generation of mixing products at IF-frequency and harmonics



■ Determination of operating point

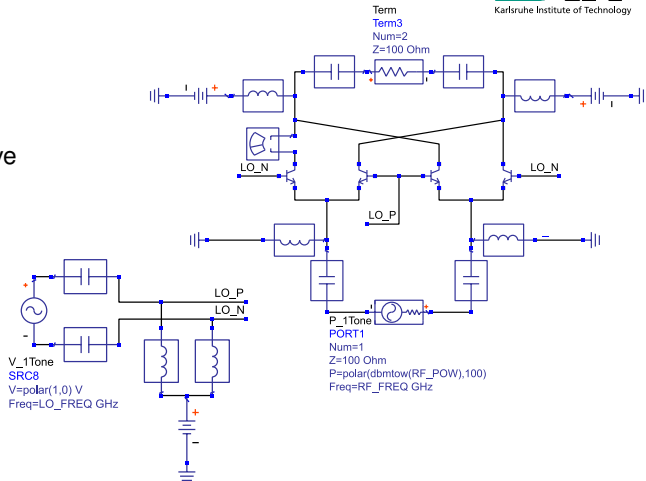- Exact value of V_{CE} not crucial
- V_{BE} : Examination of s_{21} of Large-signal s-parameter simulation and noise figure (analogous to [Mai+21])



[Mai+21] T. Maiwald et al., "A Broadband Zero-IF Down-Conversion Mixer in 130 nm SiGe BiCMOS for Beyond 5G Communication Systems in D-Band", in *IEEE Transactions on Circuits and Systems II: Express Briefs*, vol. 68, no. 7, pp. 2277-2281, July 2021

Operating Point: Switching Quad

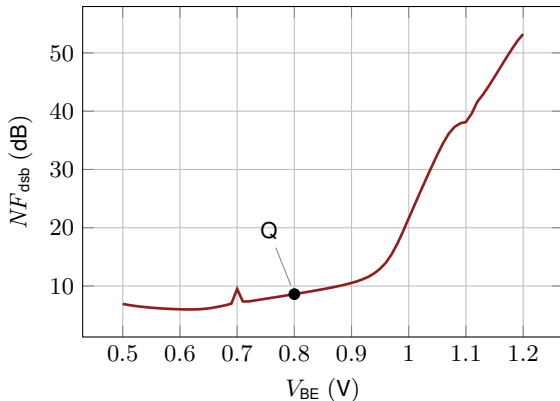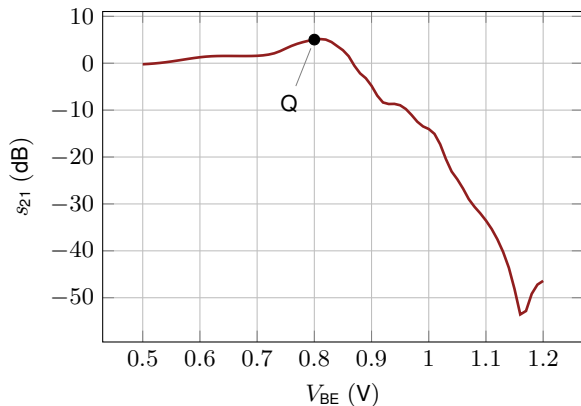

- Plotted for $f_{LO} = 135$ GHz, $f_{RF} = 140$ GHz
- Double-sideband noise figure NF_{dsb} (direct conversion mixer)
- Chosen operating point: $V_{BE} = 0,8$ V


Operating Point: Transimpedance Amplifier

■ Operation



- Conversion of switched current to voltage, amplification
- Modified Cherry-Hooper topology: decoupling of bandwidth and gain, modification for greater dynamic range

■ Determination of operating point

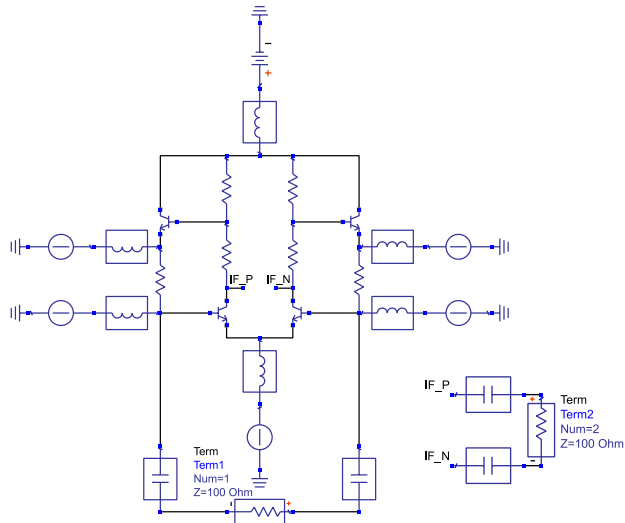- Exact value of supply voltage not crucial
- S-parameter simulation: Examination of maximum available gain (MAG) and minimum noise figure (NF_{min})
- At this stage: only determination of operating point of bottom transistors



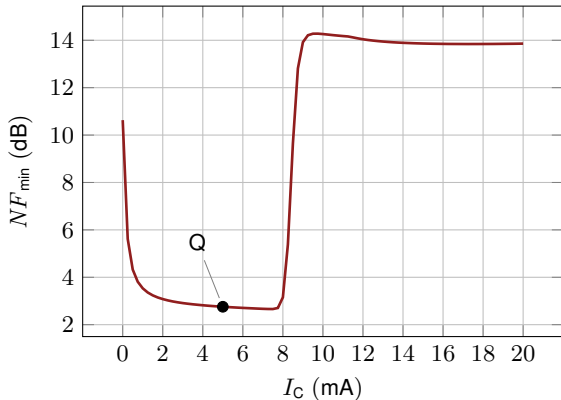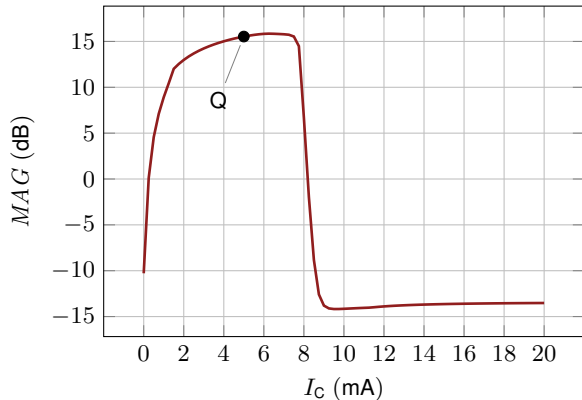Operating Point: Transimpedance Amplifier



- Plotted for $f_{IF} = 20$ GHz
- Chosen operating point: $I_C = 5$ mA (with multiplier of 10)


Operating Point: Buffer

■ Operation



- Amplification of signal
- Comprises three stages: two differential amplifiers and an emitter follower

■ Determination of operating point

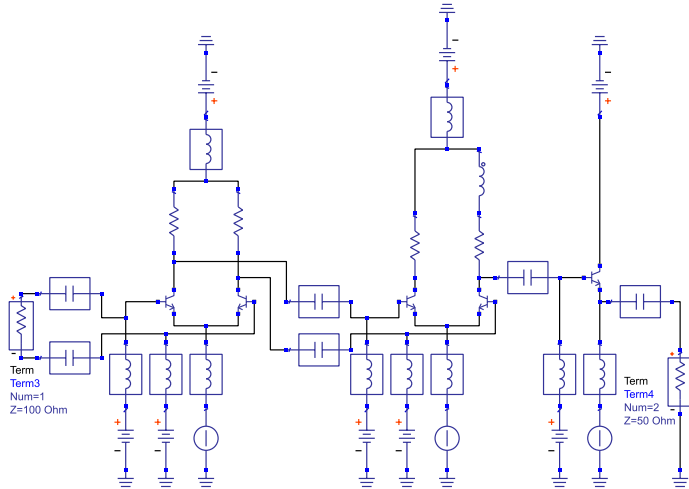- Exact value of supply voltage not crucial at this point
- S-parameter simulation: Examination of MAG and NF_{min}
- **Note:** Adjustment with respect to linearity at the very end




Operating Point: Buffer

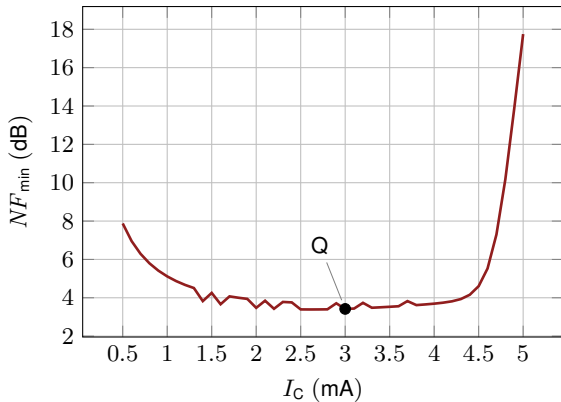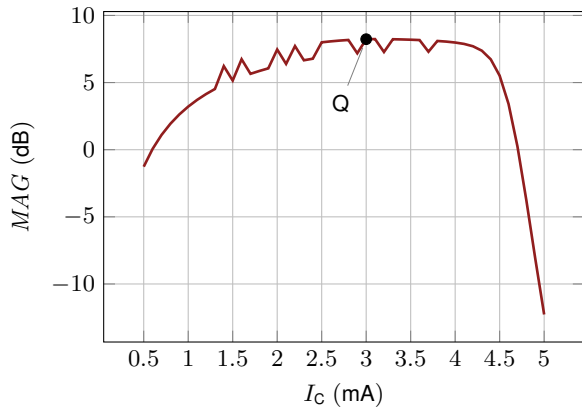





- Plotted for $f_{IF} = 20$ GHz
- Chosen operating point: $I_C = 3$ mA

Integration: SQuad & TIA

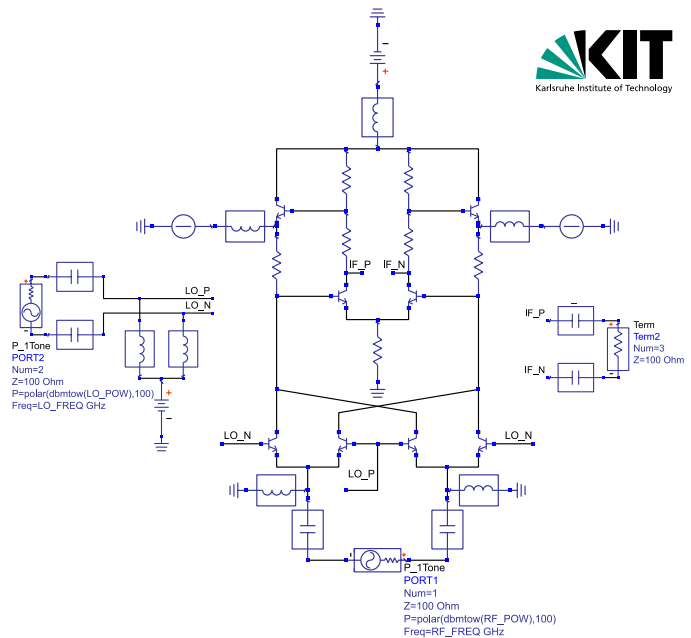- DC coupling → Redesign of bias circuitry
- Supply voltage fixed to 2,5 V to not exceed breakdown voltage of transistors
- Examination using Harmonic-Balance simulation:
 - Conversion gain
 - 1 dB compression point ($P_{1\text{ dB}}$)
 - Noise figure




Integration: SQuad & TIA

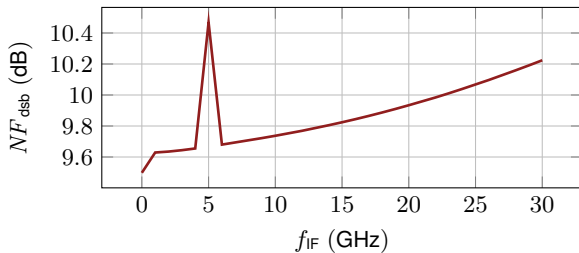
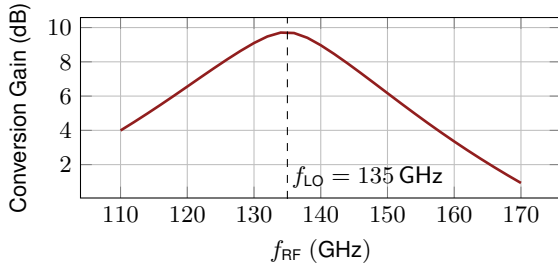
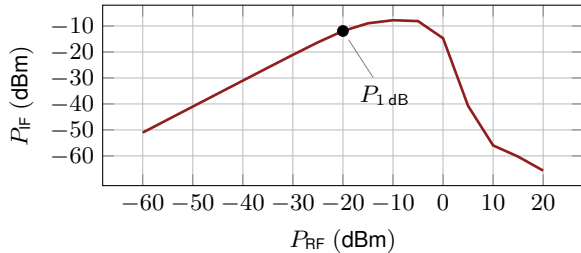
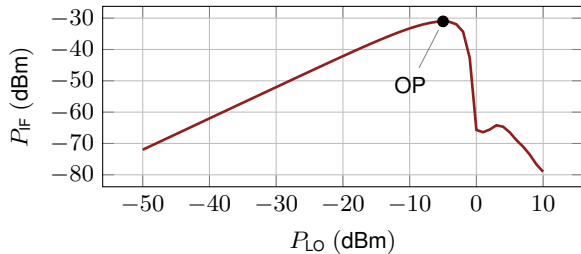


Integration: SQuad, TIA & Buffer


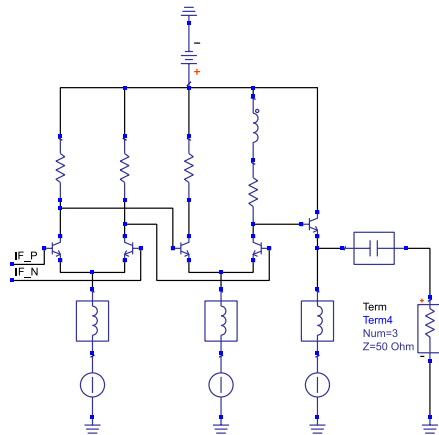
- DC coupling → Redesign of bias circuitry
- Supply voltage fixed to 2,5 V
- Examination using Harmonic-Balance simulation:
 - Conversion gain
 - 1 dB compression point ($P_{1\text{ dB}}$)
 - Noise figure







Integration: SQuad, TIA & Buffer

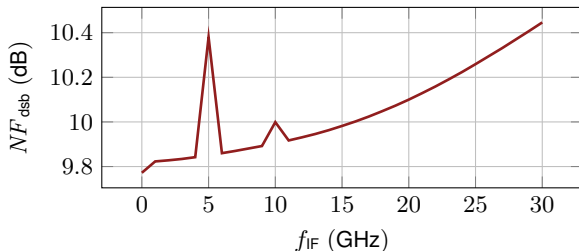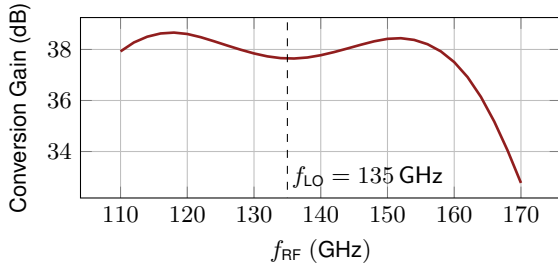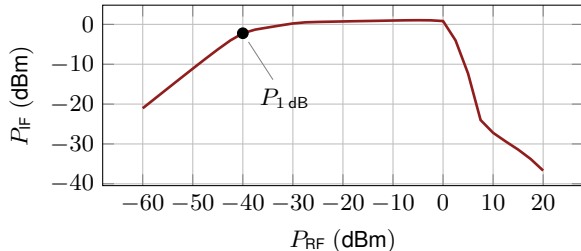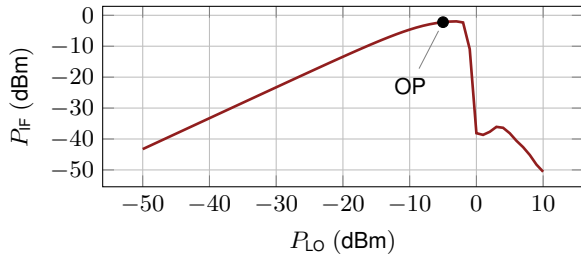

Final Circuit

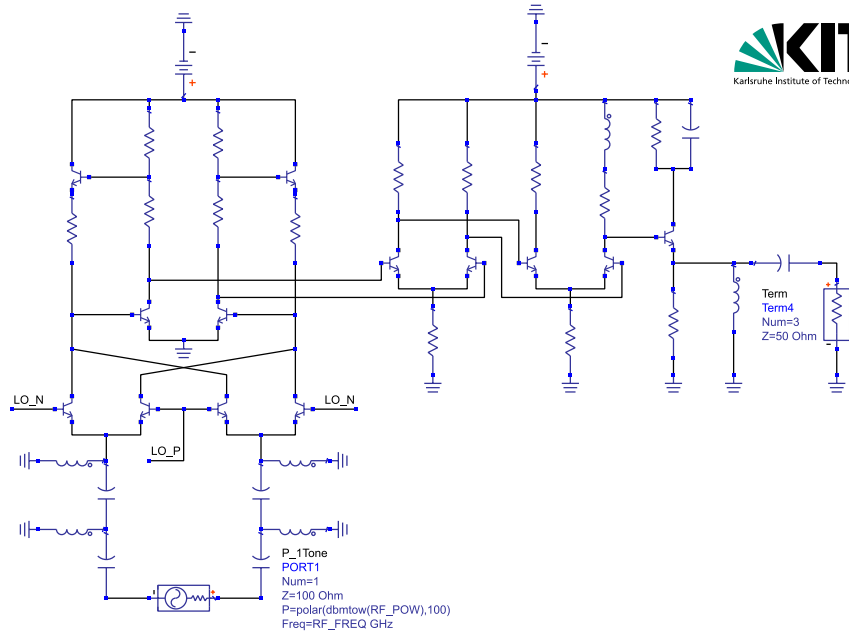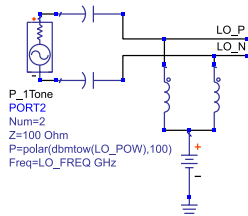

Final Circuit

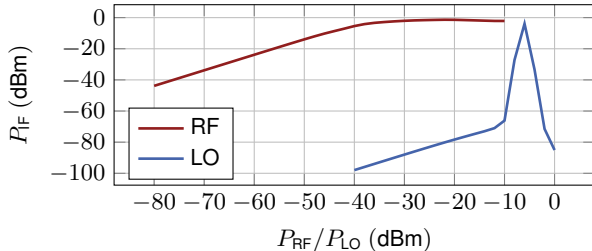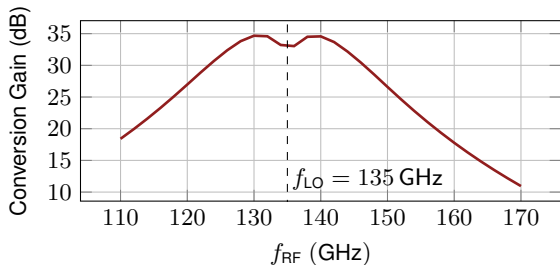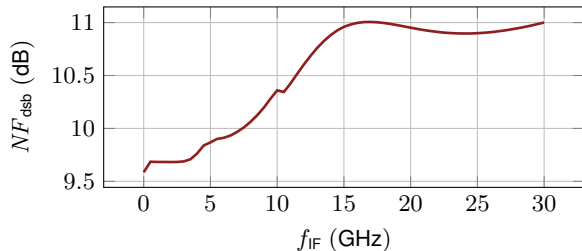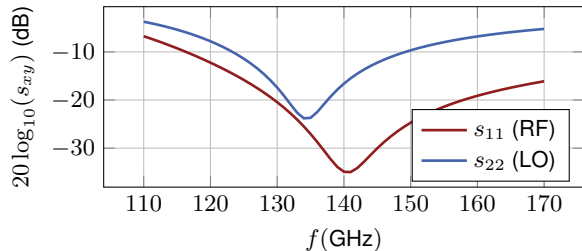

- Proposed Ideas
- Own Simulations
- Discussion & Conclusion

■ Own simulations

- Better results to be expected (technology with higher f_t , $f_{\max}$, stability not considered)
- Maybe better results by using current mirrors to set operating points of buffer instead of resistors

■ General structure

- Removal of g_m stage of Gilbert cell → more voltage headroom
- High bandwidth TIA and inductive peaking → high bandwidth
- Differential to single-ended conversion → dense chip-to-package transition

■ Applications of this design

- SiGe HBT technology integrable with CMOS → scalable, suitable for mixed-signal ICs
- Ideal for electronic beam steering in mm-Wave applications (because of small size, moderate noise figure)

Thank you for your attention!
Any questions?

